



Mark Scheme (Results)

November 2020

Pearson Edexcel International GCSE
In Physics (4PH1) Paper 1PR

Question number	Answer	Notes	Marks
9 (a)	correct voltmeter symbol; voltmeter connected in parallel with resistor;		2
(b)	light dependent resistor;	allow LDR	1
(c) (i)	9(.0) (V);		1
(ii)	substitution OR rearrangement; evaluation; e.g. $9.0 = \text{current} \times 4500$ OR $\text{current} = \text{voltage} / \text{resistance}$ (current =) 0.0020 (A)	allow ecf from (i) allow 0.002 (A)	2
(iii)	substitution OR rearrangement; evaluation in Ω ; conversion to $k\Omega$; e.g. $3.0 = 0.0020 \times \text{resistance}$ OR $\text{resistance} = \text{voltage} / \text{current}$ (resistance =) 1500 (Ω) (resistance =) 1.5 ($k\Omega$)	allow ecf from (ii)	3
(d)	lamp should be connected in parallel with component X / LDR; resistance of component X increases when it gets dark; voltage across component X increases / becomes greater than 10V when it gets dark;		3

Total for Question 9 = 12 marks

Question number	Answer	Notes	Marks
10 (a)	<p>method to show shape; e.g. use compass(es) use of iron filings/powder</p> <p>use of plotting compass to show direction;</p> <p>a further method detail; e.g. mark card/move compass/multiple compasses idea of another line or lines added sprinkle (iron filings) tap card (to distribute iron filings)</p>	all marks may be awarded from a labelled diagram	3
(b) (i)	<p>any four from: MP1. idea that core gains a magnetic field; MP2. idea of a changing magnetic field; MP3. idea that field lines cut by wire; MP4. voltage induced (across coil); MP5. (causing a) current in the wire;</p>	allow higher level ideas in terms of flux and flux linkage	4
(ii)	<p>any one from: MP1. idea that dynamo-wheel friction makes bicycle harder to pedal; MP2. idea that lights would vary in brightness;</p> <p>MP3. lights will be off when bicycle is stationary;</p>	allow current / brightness of lamps depends on how fast bicycle is moving	1

Total for Question 10 = 8 marks