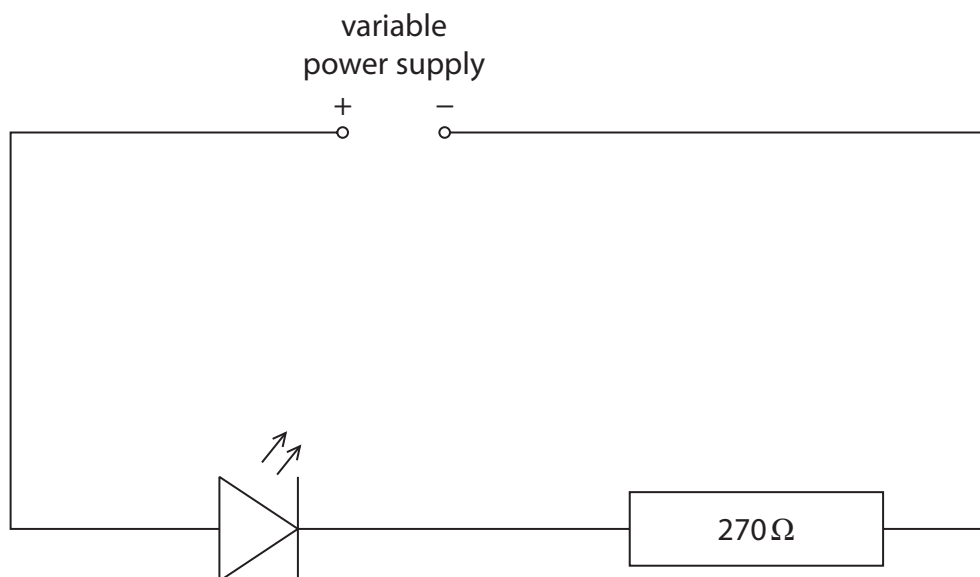


- 5 The diagram shows a circuit used to investigate the relationship between current and voltage for a light-emitting diode (LED).



- (a) Draw meters on the diagram to measure the voltage of the LED and the current in the LED. (3)

