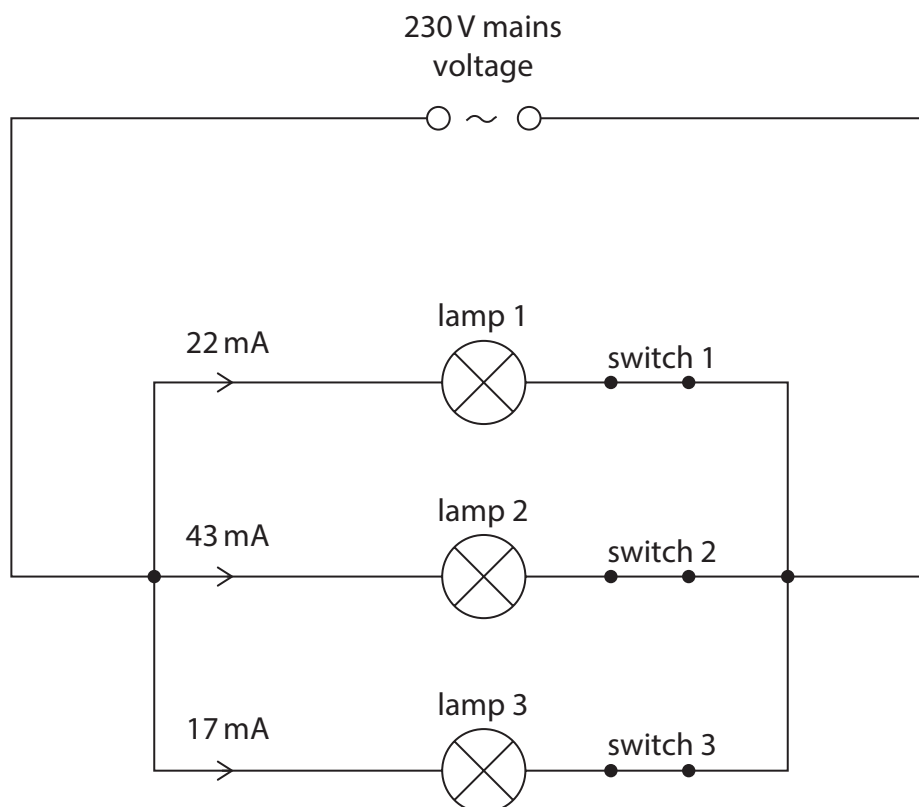


7 The diagram shows a domestic lighting circuit.



DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

(a) Explain an advantage of using this circuit for domestic lighting.

(2)

(b) When switch 1 is closed, the current in lamp 1 is 22 mA.

(i) Give the name of the charged particle that moves in an electric current.

(1)



(ii) Show that lamp 1 has a power of about 5 W.

(3)

(iii) Calculate the energy transferred by lamp 1 when it is on for 30 seconds.

(3)

energy transferred = ..... J

(c) The circuit is connected to the mains supply. Mains voltage is 230 V.

(i) State what is meant by the term **voltage**.

(1)

(ii) Switches 1 and 3 are closed, which turn on lamps 1 and 3.

Switch 2 is open.

Calculate the current in the mains supply.

(2)

current = ..... mA

**(Total for Question 7 = 12 marks)**

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA



P 7 5 8 2 6 A 0 1 7 3 2