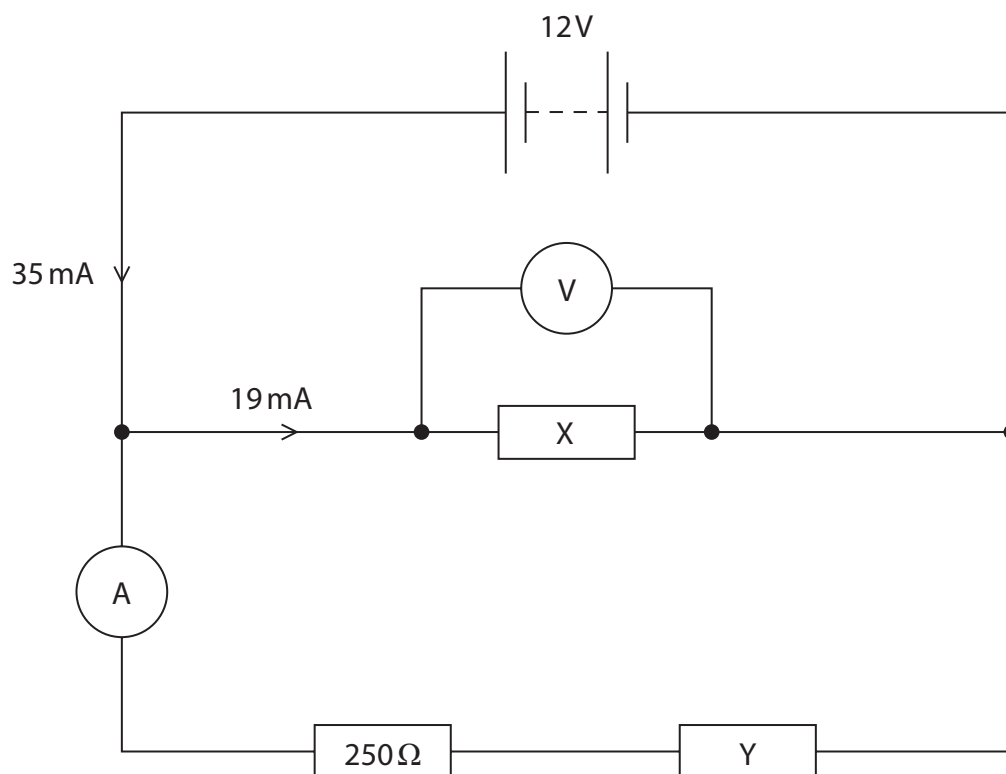


- 11 The diagram shows a circuit that includes a battery, an ammeter, a voltmeter and three different resistors.



- (a) (i) Give the voltmeter reading.

(1)

voltage = V

- (ii) State the formula linking voltage, current and resistance.

(1)

- (iii) Calculate the resistance of resistor X.

(3)

resistance = Ω



DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

(b) (i) Give the reason why the reading on the ammeter would be 16 mA.

(1)

.....

.....

(ii) Calculate the resistance of resistor Y.

(4)

resistance = Ω

(c) Resistor X and the voltmeter are removed from the circuit, leaving a break in this part of the circuit.

Explain how the current in the battery changes when these components are removed.

(2)

.....

.....

.....

.....

.....

.....

(Total for Question 11 = 12 marks)

