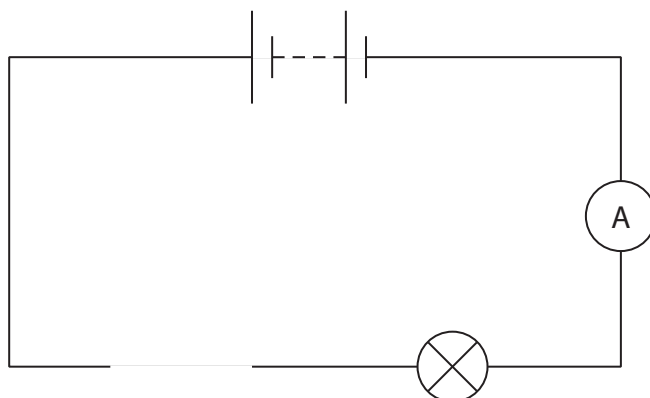


8 The diagram shows an incomplete series circuit.



DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

(a) (i) Draw a thermistor to complete the circuit.

(1)

(ii) Add a voltmeter to the circuit to measure the voltage across the lamp.

(2)

(b) The voltmeter measures a voltage of 5.6V.

The ammeter measures a current of 790 mA.

(i) State the equation linking voltage, current and resistance.

(1)

(ii) Calculate the resistance of the lamp.

(3)

resistance = .....  $\Omega$



DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

- (c) The completed circuit is moved from a cold room to a hot room.

Explain how this would affect the brightness of the lamp.

(3)

- (d) State how the current in the circuit would change if another lamp is added in series with the first lamp.

(1)

**(Total for Question 8 = 11 marks)**

