

- 5 A student sets up a circuit to investigate how the current in different components varies with voltage.

He investigates these components.

- a short thick copper wire
- a filament lamp
- a long thin copper wire
- a diode

- (a) State four other pieces of equipment the student needs.

(4)

1

2

3

4

- (b) During the investigation, the student keeps the two copper wires at a constant temperature.

- (i) Give a reason why he should keep the wires at a constant temperature.

(1)

.....

.....

.....

.....

- (ii) Describe how he could keep the wires at a constant temperature.

(2)

.....

.....

.....

.....

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA



DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

(c) The student obtains a graph for each component.


Draw a straight line linking each component to its correct graph.

(3)


component

graph


short thick
copper wire

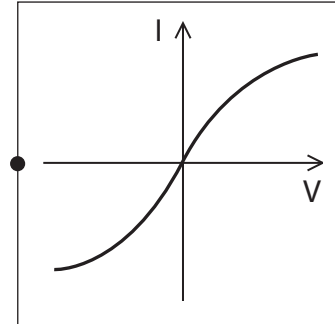


filament lamp

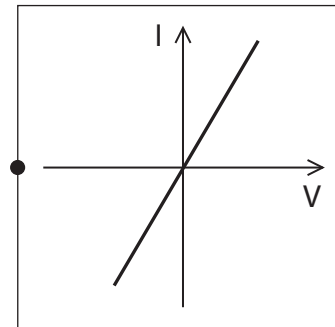

long thin
copper wire

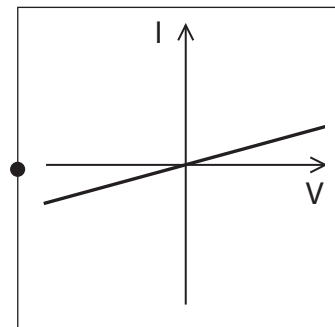

diode

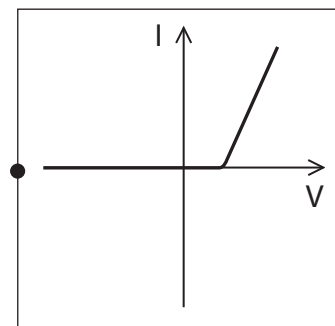

(Total for Question 5 = 10 marks)

