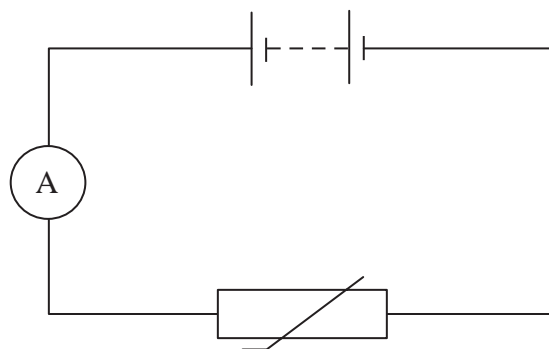


- 10** A student investigates how the resistance of a thermistor changes with temperature. He measures a current and a voltage.

The diagram shows part of the circuit that the student uses.



- (a) (i) Label the thermistor on the diagram.

(1)

- (ii) Add to the diagram to show how a voltmeter should be connected.

(2)

- (b) The student varies the temperature of the thermistor and obtains the results below.

Temperature in °C	0	20	40	60	80	100
Current in mA	0.8	2.0	4.2	8.2	15.1	26.6

- (i) State the equation linking voltage, current and resistance.

(1)

- (ii) The voltage across the thermistor is 12 V.

Calculate the resistance of the thermistor at 20 °C.


(2)

Resistance = Ω



- (iii) Use the results from the table opposite to plot a graph of current against temperature.

(5)

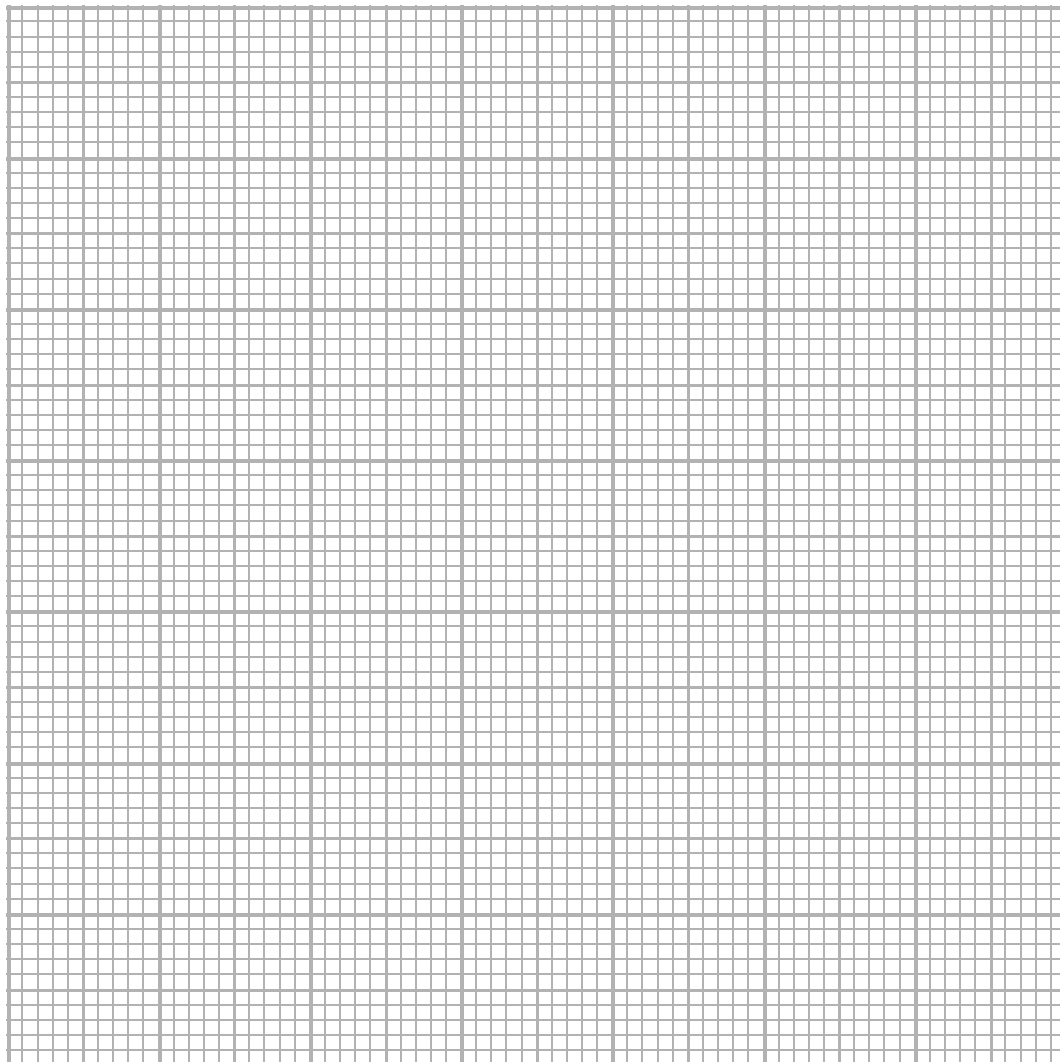

- (iv) Use your graph to describe how the current in the thermistor changes as the temperature increases.

(2)

.....

.....

.....

.....



(v) The student concludes:

As the temperature increases,
the **resistance** of the
thermistor also increases.



Evaluate this conclusion.

(2)

.....

.....

.....

.....

.....

.....

(Total for Question 10 = 15 marks)

