

Question number	Answer	Notes	Marks
6 (a)	correct symbol for voltmeter in parallel with any component; voltmeter drawn in parallel with the LDR;		2
(b) (i)	$V = I \times R$;	allow any re-arrangement allow word equation condone 'i' for current reject 'c' or 'C' for current	1
(ii)	substitution; evaluation; e.g. $V = 7.8 \times 10^{-3} \times 73$ $V = 0.57 \text{ (V)}$	POT error gives 1 mark penalty allow 0.5694 (V) for both marks '0.6 (V)' scores 1 mark	2
(iii)	idea that voltages of two resistors in series adds up to supply voltage; calculation of correct voltage; e.g. $V_{\text{cell}} = 1.5 = V_{\text{LDR}} + V_{\text{resistor}}$ $V_{\text{LDR}} = 1.5 - 0.56(94)$ $V_{\text{LDR}} = 0.93 \text{ (V)}$	allow ecf from 6(c)(ii) allow 0.9306 (V) for both marks	2
(c) (i)	resistance decreases (with increasing L.I.); non-linear/decreasing rate/curve;		2
(ii)	increases;		1
(iii)	larger current means larger voltage across fixed resistor; total voltage remains constant;		2

Total for Question 6 = 12 marks