

- 6 A washing machine has an electric motor and an electric heater.



The resistance of the heater is $22\ \Omega$.

The mains voltage is 230 V .

- (a) (i) State the equation linking voltage, current and resistance.

(1)

- (ii) Show that the current in the heater is about 10 A when it is working.

(2)



(b) The washing machine is fitted with a fuse rated at 13 A.

(i) Explain why the washing machine is fitted with a fuse.

(2)

.....

.....

.....

.....

.....

(ii) When the motor is working, the current in it is 1.74 A.

Explain why it would **not** be sensible to replace the 13 A fuse with a 2 A fuse.

(2)

.....

.....

.....

.....

.....

(Total for Question 6 = 7 marks)

