
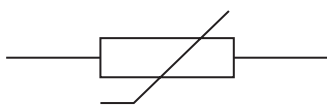


2 This question is about electricity.

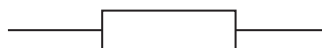
(a) The diagram shows some electrical circuit symbols.




**A**



**B**

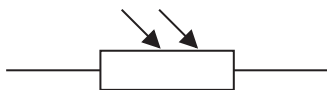

**C**

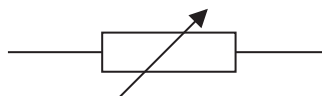

**D**

(i) Which symbol represents a light dependent resistor (LDR)?

(1)

- ☐ **A**
- ☐ **B**
- ☐ **C**
- ☐ **D**

(ii) Which symbol represents a fixed resistor?

(1)

- ☐ **A**
- ☐ **B**
- ☐ **C**
- ☐ **D**

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA



DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

DO NOT WRITE IN THIS AREA

(b) An electric heater connected to the mains supply has a power of 2200 W.

(i) State the equation linking power, current and voltage.

(1)

(ii) Show that the current in the electric heater is approximately 10 A.  
[mains supply voltage = 230 V]

(2)

(iii) Which of these fuses should be used with the electric heater?

(1)

☐ **A** 3 A

☐ **B** 5 A

☐ **C** 7 A

☐ **D** 13 A

(iv) Explain how the fuse protects the electric heater when the current in the electric heater is too high.

(2)

.....

.....

.....

.....

**(Total for Question 2 = 8 marks)**

