

- 5 A student does an investigation to determine the current-voltage graph for an unknown component, X.

The student uses this equipment

- component X
- cell
- variable resistor
- ammeter
- voltmeter
- connecting wires

- (a) Complete the circuit diagram to show how the student should set up this equipment for her investigation.

(4)

component X

